

PART C [20 MARKS]

Instruction: Answer all questions. You must show all necessary working clearly.

Figure 1 shows a schematic diagram of an LED array light. You are required to design a combinational logic circuit to be embedded into the Circuit Box.

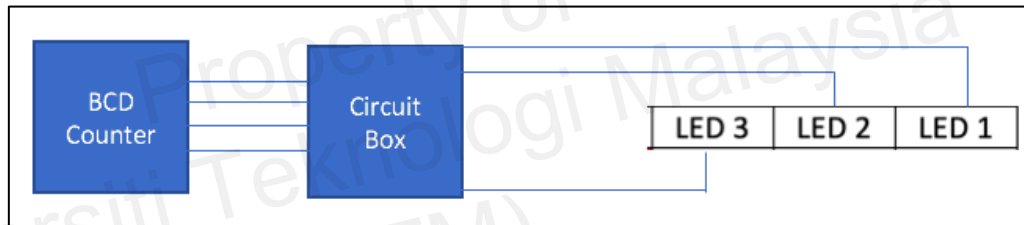


Figure 1

The Circuit Box receives a BCD sequence from a BCD counter as its input, and then lit the LED array according to Table 1.

Table 1

Decimal	LED 3	LED 2	LED 1
0			
1			
2			
3			
4			
5			
6			
7			
8			
9			

Legend:

Active High LED is OFF

Active High LED is lit



You are required to:

1. Produce the truth table that defines the function of the Circuit Box. [9m]
2. Derive the simplified SOP Boolean equation of LED1, LED2 and LED3 using K-Map. [6m]
3. Sketch the combinational logic circuit of the Circuit Box using basic gates only. [5m]