

**SULIT**



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

**SCHOOL OF COMPUTING**  
Faculty of Engineering

**UNIVERSITI TEKNOLOGI MALAYSIA**  
**FINAL EXAMINATION SEMESTER I 2019 / 2020**

**SUBJECT CODE** : SECR1013 / SCSR1013  
**SUBJECT NAME** : DIGITAL LOGIC  
**SECTION** : SECR/J/B/V/P / SCSR/J/B/V/P  
**TIME** : 3 HOURS  
**DATE/DAY** :  
**VENUES** :

---

**INSTRUCTIONS:**

Answer all questions from PART A and PART B. Show all your works.

This test will contribute 35% towards the total marks of 100%.

**(Please Write Your Lecturer Name And Section In Your Answer Booklet)**

<b>Name</b>	
<b>I/C No.</b>	
<b>Year / Course</b>	
<b>Section (Circle)</b>	<b>01 / 02 / 03 / 04 / 05 / 06 / 07 / 08 / 09</b>
<b>Lecturer Name (Circle)</b>	<b>Mr Firoz / Mrs Zuriahati / Mrs Rashidah</b>

This question paper consists of 16 printed pages excluding this page.


## **PART A: OBJECTIVES**

**Answer ALL questions in answer booklet.**

1. What is a multiplexer?
  - A. It is a type of decoder which decodes several inputs and gives one output.
  - B. A multiplexer is a device that has many inputs and a single output.
  - C. It takes one input and results into many outputs.
  - D. It is a type of encoder which decodes several inputs and gives one output.
  
2. How many outputs are in a BCD decoder?
  - A. 4
  - B. 5
  - C. 15
  - D. 10
  
3. In 1-to-4 demultiplexer, how many select lines are required?
  - A. 2
  - B. 3
  - C. 4
  - D. 5
  
4. In a multiplexer the output depends on its \_\_\_\_\_.
  - A. data outputs
  - B. select inputs
  - C. select outputs
  - D. rotate pin

5. Parity generators/checkers use which modulo summation?
- A. Modulo 8
  - B. Modulo 16
  - C. Modulo 2
  - D. Modulo 10
6. A code converter is a logic circuit that \_\_\_\_\_.
- A. Inverts the given input
  - B. Converts into decimal number
  - C. Converts data of one type into another type
  - D. Converts to hexadecimal
7. Which of the following is NOT a latch?
- A. S-R latch
  - B. T latch
  - C. Gated S-R latch
  - D. Gated D latch
8. The invalid state of active HIGH S-R latch occurs when \_\_\_\_\_.
- A.  $S = 1, R = 0$
  - B.  $S = 0, R = 1$
  - C.  $S = 1, R = 1$
  - D.  $S = 0, R = 0$

 9. The diagram below shows what type of temporary storage device?



- A. D flip flop
  - B. C-D flip flop
  - C. Gated S-R latch
  - D. Gated D latch
10. Which of the following is considered as highest priority asynchronous input(s)?
- A. Clock
  - B.  $\overline{PRE}$
  - C. T
  - D. J and K
11. When both inputs of a J-K pulse-triggered flip-flop are HIGH, and the clock triggers, what will the output be?
- A. An invalid state will exist.
  - B. No change will occur in the output.
  - C. The output will reset.
  - D. The output will toggle.
12. Which statement is FALSE regarding universal bidirectional shift register (74HC194)?
- A. Can implement Serial In Serial Out (SISO) operation
  - B. Can implement Serial In Parallel Out (SIPO) operation
  - C. Can implement Parallel In Serial Out (PISO) operation
  - D. Can implement Round Robin In Parallel Out (RRPO) operation

13. A modulus 16 ring counter requires how many flip-flops?
- A. 2
  - B. 4
  - C. 8
  - D. 16
14. If a 10-bit ring counter has an initial state 1101000000, what is the state after the third clock pulse?
- A. 1101000000
  - B. 0001101000
  - C. 1100000000
  - D. 0000000000
15. A modulus 12 Johnson counter requires a minimum of \_\_\_\_\_.
- A. 10 flip-flops
  - B. 12 flip-flops
  - C. 6 flip-flops
  - D. 2 flip-flops
16. On the third clock pulse, a 4-bit Johnson sequence is  $Q_0 = 1$ ,  $Q_1 = 1$ ,  $Q_2 = 1$ , and  $Q_3 = 0$ . On the fourth clock pulse, the sequence is \_\_\_\_\_.
- A.  $Q_0 = 1$ ,  $Q_1 = 1$ ,  $Q_2 = 1$ ,  $Q_3 = 1$
  - B.  $Q_0 = 1$ ,  $Q_1 = 1$ ,  $Q_2 = 0$ ,  $Q_3 = 0$
  - C.  $Q_0 = 1$ ,  $Q_1 = 0$ ,  $Q_2 = 0$ ,  $Q_3 = 0$
  - D.  $Q_0 = 1$ ,  $Q_1 = 0$ ,  $Q_2 = 0$ ,  $Q_3 = 0$
17. An asynchronous counter differ from a synchronous counter in \_\_\_\_\_.
- A. the number of states in its sequence
  - B. the type of flip flop used
  - C. the method of clocking
  - D. the value of modulus

18. A modulus-12 asynchronous counter must have \_\_\_\_\_.
- A. 12 flip-flops
  - B. 4 flip-flops
  - C. 3 flip-flops
  - D. 5 flip-flops
19. Four cascaded modulus-10 counters have an overall modulus of \_\_\_\_\_.
- A. 40
  - B. 10
  - C. 1000
  - D. 10000
20. Which asynchronous counter mod is a truncated sequence?
- A. mod 4
  - B. mod 8
  - C. mod 13
  - D. mod 16

## **PART B: STRUCTURED**


**Answer ALL questions in question and answer booklet.**

### **Question 1 [16 Marks]**

- a) Draw the block diagram for a 3-bit parallel adder using full adder and label clearly the block diagram including the input, sum and carry. Perform addition  $011_2 + 110_2$ , show the value for each label on the block diagram. [4]

$$\begin{array}{r} A_3 \ A_2 \ A_1 \\ + \ B_3 \ B_2 \ B_1 \\ \hline \sum_4 \sum_3 \sum_2 \sum_1 \end{array}$$


- b) For set of binary numbers  $A_3A_2A_1A_0 = 0010$   $B_3B_2B_1B_0 = 0101$  are assigned to comparator in Figure 1.

 

**Figure 1**

- Based on Figure 1, explain how comparator works until final output results appear. [3]
- Determine the final output result for the comparator in Figure 1. [1]

- c) Given an active HIGH 7-segment display in Figure 2 showing a digital number from a decoder that is based on the BCD value, **complete Table 1 in your question booklet APPENDIX A.** [4]

 

**Figure 2**

- d) Figure 3 in APPENDIX A shows DEMUX connection with outputs labelled as  $Y_3$   $Y_2$   $Y_1$   $Y_0$  and B is the input of DEMUX. Select bit for DEMUX are noted by  $C_1$  and  $C_0$  ( $C_1$  is the MSB). **Draw the waveform for the DEMUX output based on the given values in question booklet Figure 3 APPENDIX A.** [4]

### **Question 2 [15 Marks]**

- a) Draw the output Q for a positive edge triggered D flip flop and assume initial Q is LOW. **Draw the waveform in question booklet Figure 4 APPENDIX A.** [4]
- b) Complete Table 2 based on the output for all Q in Figure 4. **Complete Table 2 in your question booklet APPENDIX A.** [3]
- c) Assume that Q is initially LOW, for gated S-R latch. **Draw the waveform for output Q in question booklet Figure 5 APPENDIX A.** [3]
- d) Determine output Q in Figure 6 for a positive edge triggered JK flip-flop with  $\overline{\text{PRE}}$ ,  $\overline{\text{CLR}}$ , and J, K inputs. Assume that Q is initially LOW. **Draw the waveform in question booklet Figure 6 APPENDIX A.** [5]



### **Question 3 [18 Marks]**

Design a synchronous counter to produce the following binary sequence:


- 0, 9, 1, 8, 2, 7, 3, 6, 4, 5, 0, 9... (recycle counter)
- Positive edge flip-flops
- Using T flip-flops, use  $Q_0$  as LSB

- a) Create state diagram [3]
- b) Develop the next state table and flip-flops transition table. [6]
- c) Determine the Boolean expression using K-Map. [4]
- d) Draw the circuit. [5]

### **Question 4 [16 Marks]**

- a) An asynchronous counter with the following specification: [7]
  - Recycle count up from 0 to 5
  - Negative edge flip-flops
  - Using JK flip-flops, use  $Q_0$  as LSB
- i. Determine the number of flip-flops required.
- ii. Design an active low decoder (NAND) for the asynchronous counter.
- iii. Draw the circuit connection for the asynchronous counter.

b) Analyze the following circuit as shown in Figure 7. [9]

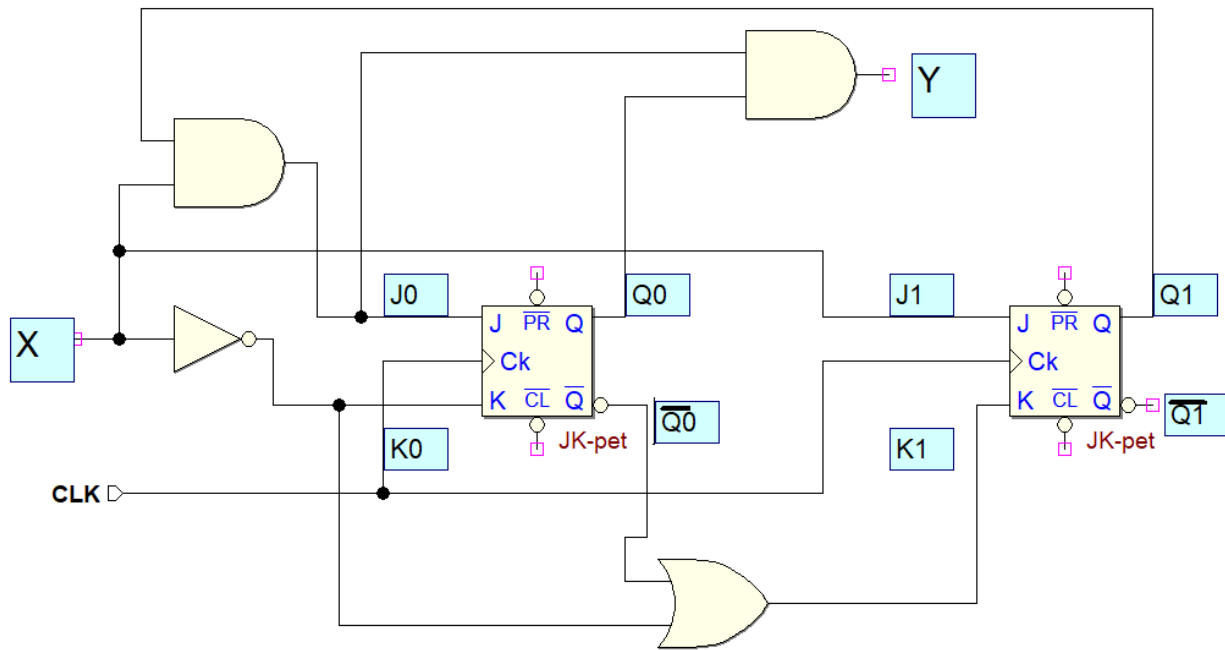

**Figure 7**

i. Derive Boolean expression for the J0, K0, J1, K1 and output Y.

ii. Use Method 2 to produce the next state and flip flop transition table. Use the following Table 3 header.

**Table 3**

Input	Present State		Next State		JK FF Transition				Output
X	Q1	Q0	Q1+	Q0+	J1	K1	J0	K0	Y

iii. Draw a complete state diagram for the circuit shown.

**Question 5 [15 Marks]**

a) A helpful analogy for a shift register is a conveyor belt. As illustrated in Figure 8 (i), (ii) and (iii) showing a single conveyor belt at four different times and determine which of the following shift register operations the sequence represents. Justify your answer. [4.5]


Answer options:

Parallel-in, serial-out

Serial-in, serial-out

Parallel-in, parallel-out

Serial-in, parallel-out

 

**Figure 8**

b) Draw and label clearly the logic diagram for 5 bit SISO (serial in serial out) shift register circuit using D flip flops. [4]

c) For 6 bit SIPO (serial in parallel out) shift register, [4]

- i. Complete Table 4 header in answer booklet for 6 clock cycles. The following 6 bit data is used with MSB entered first.

**Q5**
**1**
**0**
**0**
**0**
**Q0**
**1**

**Table 4**

Clock	FF0	FF1	FF2	FF3	FF4	FF5
Initial	0	0	0	0	0	0

- ii. At what clock cycle can all the input data be read at the output?

d) Draw the output waveform  $Q_4$  of a 5-bit PISO (parallel in serial out) shift register if the data input entered is  $D_4D_3D_2D_1D_0 = 11001_2$ .  $D_4$  represents MSB and it will be shifted out first. **Draw the waveform in question booklet Figure 9 APPENDIX A.** [2.5]

## **APPENDIX A**

<b>NAME</b>			
<b>METRIC NO.</b>		<b>SECTION</b>	

### **Question 1**

c)


**Table 1**

BCD Input				Segment Output							Display
A	B	C	D	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>	
											3
											6
1	0	0	0								8

**APPENDIX A**

<b>NAME</b>			
<b>METRIC NO.</b>		<b>SECTION</b>	

d)

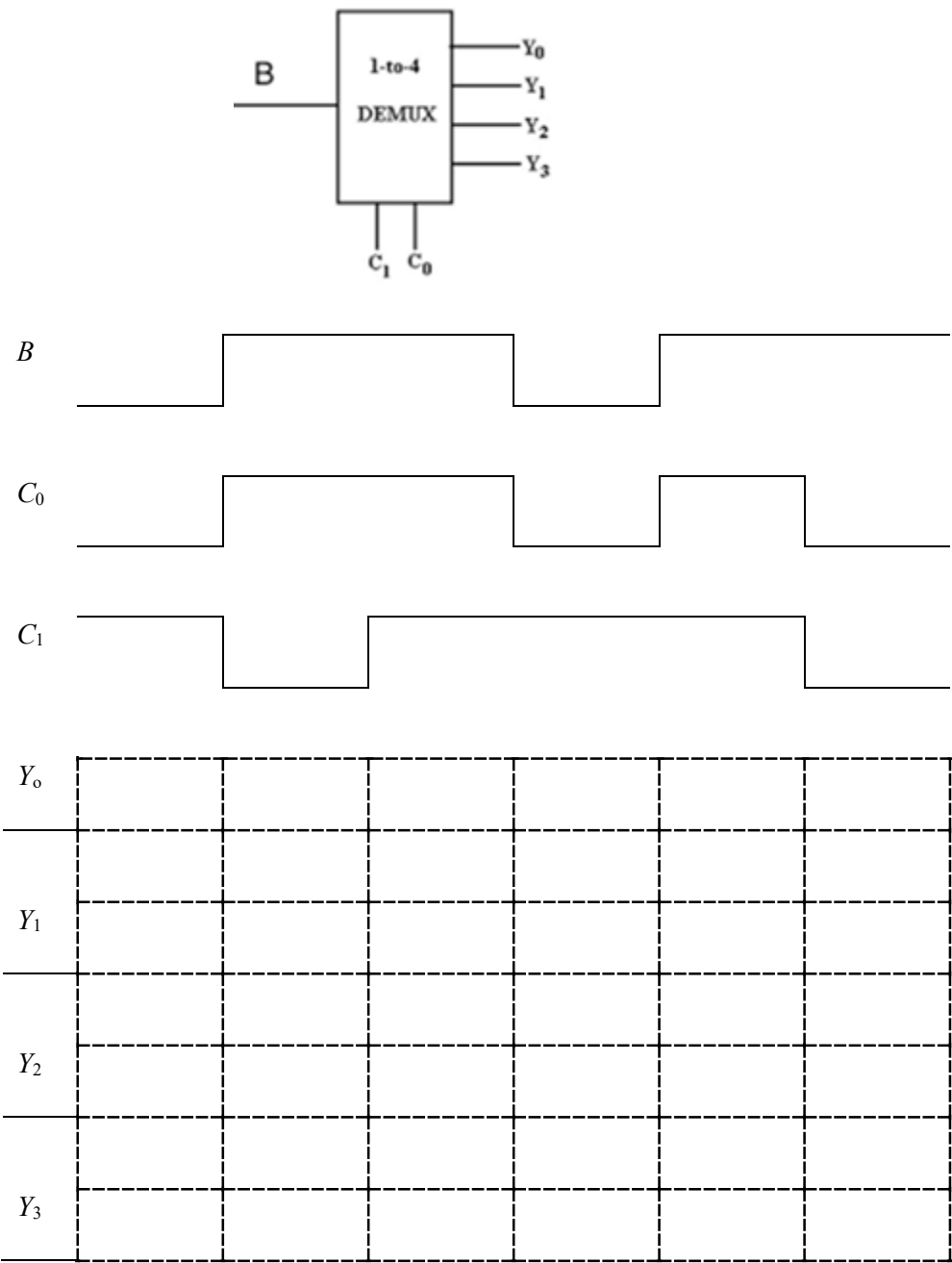


**Figure 3**  
**13**

## APPENDIX A

NAME			
METRIC NO.		SECTION	

### Question 2

a)

 

**Figure 4**

b)


**Table 2**

Clock Pulse (1 to 7)	$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	D	FF State	Mode (Async/Sync)
	X	1			
	1	X			

## APPENDIX A


NAME			
METRIC NO.		SECTION	

c)

 

**Figure 5**

d)

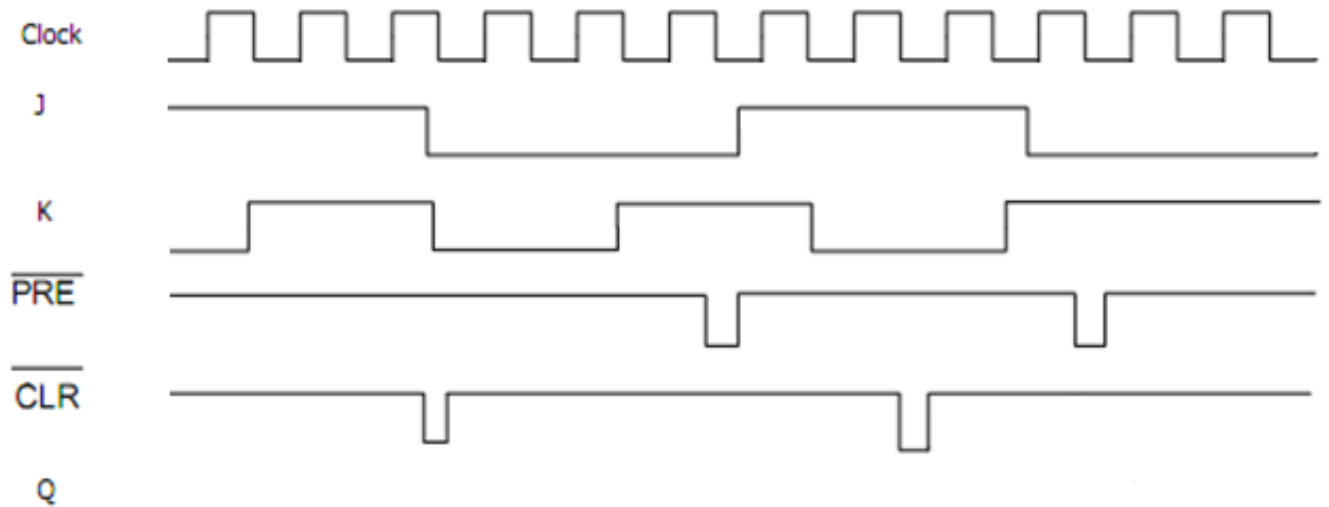

**Figure 6**




## APPENDIX A

NAME			
METRIC NO.		SECTION	

### Question 5

d)

 

**Figure 9**