SECR1013-00 DIGITAL LOGIC VIRTUAL EXAM HALL

Dashboard

My courses

SECR1013-00

TEST 2 PART A (22 MAY 2021)

TEST 2 PART A [55 marks]

Preview

Quiz navigation

ARSHAD 8739

MARINA BINTI MD

You can preview this quiz, but if this were a real attempt, you would be blocked because: This quiz is not currently available

Get the SOP and don't care notation from the following truth table.

Question 1 Not yet answered Marked out of

 Flag question Edit question

Α	В	С	D	Т
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	Х
0	1	1	1	0
1	0	0	0	Χ
1	0	0	1	Χ
1	0	1	0	Х
1	0	1	1	Х
1	1	0	0	Х
1	1	0	1	1

1

1 1

 $T = \sum_{ABCD} (1,4,12,13,15) + d(3,4,5,6,7,9)$

Select one:

1

0

0

 $T = \prod_{ABCD} (0,2,3,7,14) + d(6,8,9,10,11,12)$

 $T = \sum_{ABCD} (1,4,5,13,15) + d(6,8,9,10,11,12)$

- $T = \prod_{ABCD} (1,4,5,13,15) + d(3,4,5,6,7,9)$

a keypad to binary bit sequence?

Not yet answered

Question 2

Marked out of 1.00 Flag

Encoder

Select one:

question 袋 Edit

Binary Adder Multiplexer

Select one:

Select one:

Comparator

- question
- Question $\bf 3$

Not yet answered

Marked out of 1.50 Flag question

question

AND gate is used to produced active-low encoder. 3-bit input binary encoder is called 3 to 1 decoder.

An encoder should have only one active output at a time.

A BCD encoder should have 4 outputs.

Which of the following is a TRUE statement about the encoder function?

Which of the following functions should be used to convert the input signal of

Which functions are the most common functions required for a digital logic circuit to determine whether the car park is full or not?

Demultiplexer (Wrong answer but bonus marks for this question)

Omparator. (Correct answer but bonus marks for this question)

answered Marked out of 2.00 Flag question

Question 4

Not yet

鈴 <u>Edit</u>

question

Question 5

Marked out of

Not yet answered

2.00

Flag

question

€ Edit question Parity Generator (Wrong answer but bonus marks for this question)

Get the simplified logic expression of $P = \sum_{XYZ} (2,5,7) + d(0,4)$

Adder (Correct answer but bonus marks for this question)

 $\bigcirc P = XZ + \bar{X}\bar{Z}$

 $\bigcirc P = (X+Z)(\bar{X}+\bar{Z})$

 $\bigcirc P = XZ + X\bar{Z}$

В

Get the Boolean expression for the following logic circuit.

 $\bigcirc P = (X+Z)(X+\bar{Z})$

1.50 Flag question € Edit question

Question 7

Not yet answered


question

€ Edit

Marked out of

Question **6**

Not yet answered

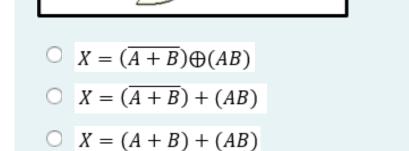

 $\bigcirc X = (\bar{A} + B) \oplus (\bar{A}B)$


Marked out of 2.00 В Flag


 \mathbf{B}

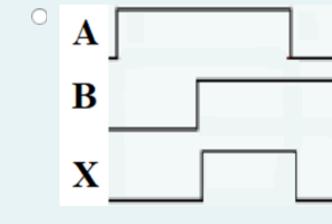question

Select one:

Determine the timing diagram of the following logic circuit.



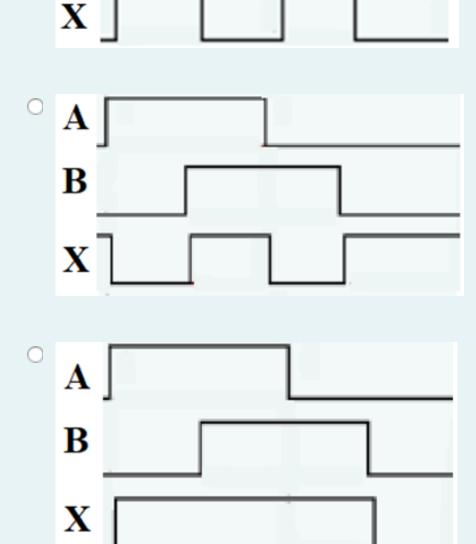

question

Question 9

Marked out of

Marked out of

1.50

Not yet answered

1.00

 Flag question

€ Edit question

Question 8

Marked out of


Not yet answered

1.50

Flag

question

₩ Edit

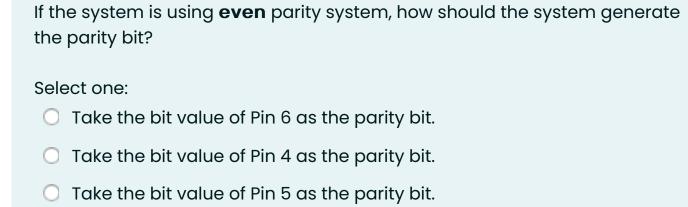

A system is using 74LS280 as its parity generator module as shown below.

The following steps are used in designing combinational logic circuit EXCEPT:

Select one:

(9)

(10) (11)

(12)

(13)

74LS280

(5) Σ Even

(6) Σ Odd

 Understand the problem to be solved Using K-Map to get the simplified Boolean expression

Draw the circuit using memory elements such as flip-flops Convert the problem statement to truth table

Take the bit value of Pin 2 as the parity bit.

Question 10 Assuming 3-bit input binary numbers $A = A_2A_1A_0$ and $B = B_2B_1B_0$, where A_2 and B_2 are MSB. Which bit is NOT the results of a 3-bit parallel adder? Not yet answered

 Flag question ○ Sum₀ Edit <u>question</u>

- O Sum₂ CarryOut₂

CarryOut₀

Jump to...

TEST 2 PART B QUESTION [15 marks] (hidden) ▶

Next page

Next activity

◀ Retest TEST 2 (hidden)

Previous activity

http://utmlead.utm.my/

□ Data retention summary

Stay in touch

!≡

Ŋ

 Ω

(~)

命

 $\bigcirc X = \bar{A}\bar{B} + AB$

Choose the FALSE statement(s) about a DECODER function.

Marked out of 1.50 Flag question € Edit

question

鈴 <u>Edit</u> question

Question 15

Not yet answered

> A decoder should have only one active output at a time. AND gate is used to produce an active low decoder

Select one or more:

3-bit input binary decoder is called 3 to 1 decoder ☐ A BCD decoder have 4-bit input and 16 possible outputs.

Question 16 Based on the following timing diagram, get the Boolean expression of output Not yet C with its inputs of A and B. answered Marked out of 1.50 Flag question

C Select one:

A + B

 $\bigcirc \overline{A+B}$

 $\bar{A} + B$

 \bigcirc $A + \bar{B}$

Select one:

XOR

NAND

answered Marked out of 1.00 Flag

Question 17

Not yet

question NOR ₩ Edit

question

XNOR

Question 18 Not yet answered

Marked out of

1.00

Flag

question

€ Edit question AND-OR logic NAND-NOR-Invert logic

POS expression is implemented by which type of logic?

Which gate is used for inequality comparison?

NAND-NOR logic

AND-OR-Invert logic

HIGH.

1.50 Flag question tib3 <u>question</u>

Question 19

Not yet

answered

Marked out of

AND

NAND

□ XOR

NOR

Select one or more:

Question 20

How many data select bits is required for a multiplexed transmission with 4 different bit streams?

 Flag question question

Not yet

answered

Marked out of

Select one: 3 bits

\$

Select logic gates that will produce LOW output when all of its inputs are

2 bits 4 bits

8 bits

Previous activity

◆ Retest TEST 2 (hidden)

Jump to...

Next activity TEST 2 PART B QUESTION [15

Next page

marks] (hidden) ▶

Stay in touch

UTM Academic Leadership - UTMLead http://utmlead.utm.my/

 Mobile: +6075537914 □ elearning@utm.my

Preview

Quiz navigation MARINA BINTI MD **ARSHAD 8739** 5 3

26

31

Finish attempt ... Start a new preview

[] Get the mobile app

!≡

Ŋ

 Ω

(~)

命

 \bigcirc

SECR1013-00 DIGITAL LOGIC VIRTUAL EXAM HALL

Dashboard

My courses

SECR1013-00

TEST 2 PART A (22 MAY 2021)

TEST 2 PART A [55 marks]

Preview

Quiz navigation

ARSHAD 8739

17

27

32

37

Finish attempt ...

16

31

MARINA BINTI MD

3

8

13

18

28

33

38

Start a new preview

14

19

29

34

39

5

10

15

20

30


35

40

You can preview this quiz, but if this were a real attempt, you would be blocked because:

This quiz is not currently available



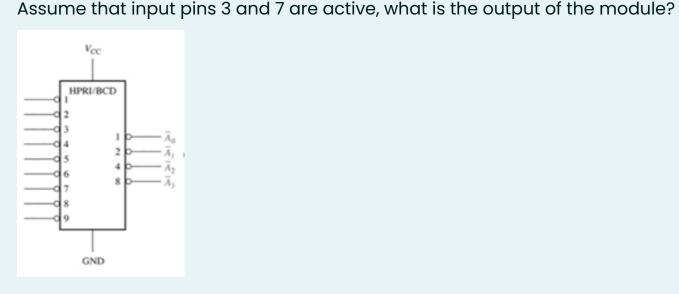

- 0 1010
- 0101
- 0011
- 0 1000

Question 22 Not yet answered

Marked out of 2.00

 Flag question € Edit <u>question</u>

Refer to the following standard SOP and POS expressions. $P = ABC + \bar{A}BC + \bar{A}B\bar{C}$

$$Q = (A + B + C)(\bar{A} + B + C)(\bar{A} + B + \bar{C})$$

What is the binary representation of the third product term? What is the binary representation of variable A in the second

Choose... \$

Choose... \$

Question 23 Not yet answered

Marked out of 1.00 Flag

question € Edit question

combination of bits on its inputs? Multiplexer

Which function should be used to detect the presence of a specified

Encoder

Decoder

Parity Checker

Question 24 Not yet answered Marked out of 1.50

₩ <u>Edit</u> question $X = \bar{A}BCD + \bar{A}\bar{B}C\bar{D} + ABC\bar{D}$

Choose the binary representations that do NOT exist in the expression,

 Flag Select one or more: question 1000

- O111
 - 1110
 - 1101

0010

Not yet answered Marked out of

Question 25

1.50

 Flag question € Edit

<u>question</u>

Select one or more:

Which of the following statement(s) is/are false?

If pin 5 and pin 7 are actives at the same, priority encoder will recognize

- pin 5 only. Look-Ahead-Carry Adder is slower than Ripple-Carry Adder.
- □ BCD to 7-segment decoder is also a type of code converter.
- BCD encoder can produce 16 codes only.

How many full adders is required to construct the parallel adder?

Not yet answered Marked out of 1.00

 Flag question

Question 26

€ Edit

Two binary values $A = 101_2$ and $B = 010_2$ will be added using a parallel adder.

- 0 3
- 0 2
- 0 4 question

Question 27 Not yet answered Marked out of

1.50

 Flag question Edit

Can act as 1 or 0 to make the group bigger. Help to produce simpler expression.

Identify the TRUE statement(s) of don't care, X

Determine the expression of distributive law.

A representation of false condition.

☐ Help to maintain the output of 1 for POS. question

Select one or more:

Question 28 Not yet answered Marked out of

1.00

 Flag question

€ Edit question

- $\bigcirc \quad A\bar{B}C + \bar{A}\bar{B}\bar{C} = \bar{B}(AC + \bar{A}\bar{C})$
- \bigcirc $A\bar{B}C = C\bar{B}A$
- $\bigcirc A + (\bar{B} + C) = (A + \bar{B}) + C$


Select one:

Marked out of 1.00 Flag question Edit question

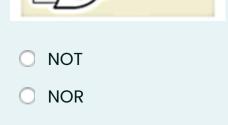Question 29

Not yet answered

What is the equivalent basic gate for the following universal circuit?



- AND OR
- - Assuming A and B are two binary values. Which of the following is NOT an output of a comparator function?

1.00 Flag question € Edit <u>question</u>

Marked out of

Question 30

Not yet

answered

○ A=B

A>B A<B</p>

○ A!=B

Jump to...

Next activity TEST 2 PART B QUESTION [15 marks] (hidden) ▶

Next page

Previous activity

◀ Retest TEST 2 (hidden)

Stay in touch UTM Academic Leadership - UTMLead

% Mobile: +6075537914

http://utmlead.utm.my/

✓ elearning@utm.my



□ Data retention summary

Get the mobile app

!≡

Ŋ

 Ω

(?)

命

Preview

MARINA BINTI MD

9

14

19

24

29

34

3

8

13

18

23

28

33

17

27

32

5

10

15

20

25

30

35

Stay in touch